

IE 1206 Embedded Electronics

Charge Q-Coulomb (C)
 Atoms have protons & neutrons & electrons.
 Protons and electrons have charge (measured in coulombs).

force $\hookrightarrow F = k \frac{Q_1 Q_2}{r^2}$
 constant k , Q_1, Q_2 charge, r^2 dist from Q_1 to Q_2
 opposite attract, similar repel.

Current I-Ampere (A)
 Flow of charge per second through a cross-section.

$I = \frac{dQ}{dt}$
 change in charge / change in time
 current

Electric Potential V-volt (V)
 Potential energy of a charge in an electric field

$V = \frac{PE}{q}$
 Potential Energy / charge
 Electric Potential

Resistance R-Ohm (Ω)

Some materials restrict the flow of charge.

Electric potential $\hookrightarrow V = IR$
 current, Resistance

Property of the material

$R = \rho \frac{L}{A}$
 length, Area, Resistivity
 silver 1.6×10^{-8} , glass 10^9

Power P-Watt (w)

Rate that electrical energy is transferred into other form of energy

$P = \frac{E}{t} = \frac{QV}{t} = IV$
 Electric potential, current
 $P_{delivered} = P_{consumed}$


$P > 0 \Rightarrow$ Power is consumed
 $P < 0$ Power is delivered to the circuit

Circuit Elements



Resistor:



Independent Voltage:

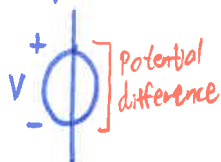


Independent Current:

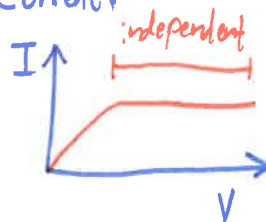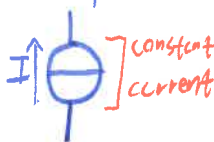



Kirchoff's Current law

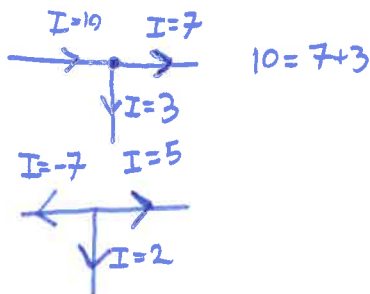All charge flowing into a node also flows out of the node.



Kirchoff's Voltage law

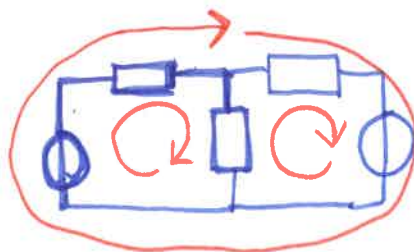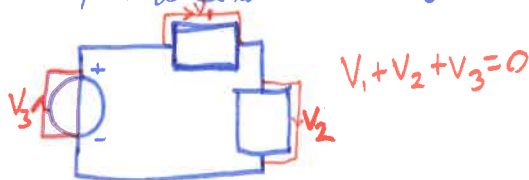The sum of all voltage elements in a loop is equal to zero.




Node Voltage Method

1. Assign a potential to every node in circuit.
2. Assign ground to one of the nodes.
3. Use KCL to express current in terms of node potentials.
4. solve equations & determine potentials.

Current Mesh Method

1. Assign current to all loops in circuit
2. Use KVL to express voltages in terms of the currents.
3. solve equations & determine the currents.

Thévenin Equivalent Circuits

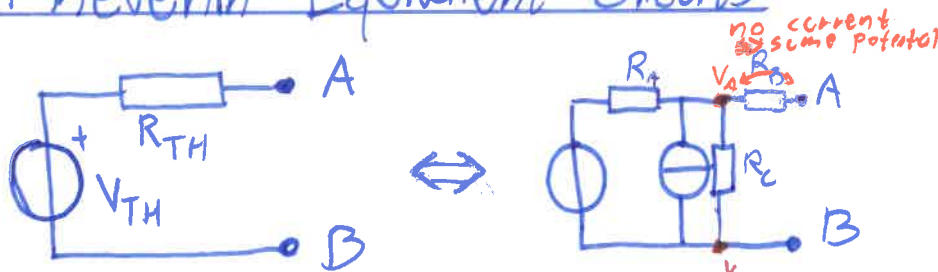


$$R_{TH} = \text{Total resistance}_{A \text{ to } B} = R_B + \frac{1}{\frac{1}{R_A} + \frac{1}{R_C}}$$

$$V_{TH} = \text{voltage difference}_{A \text{ to } B} = V_A - V_B$$


Diodes

Allows current in a single direction.

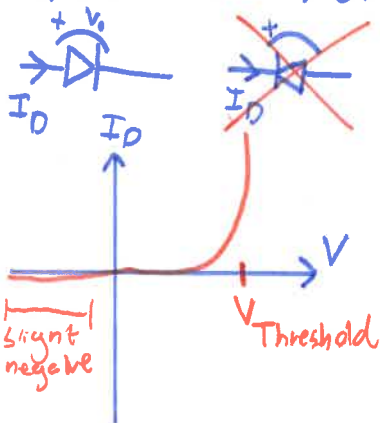


Real

$$I_D = I_S (e^{\frac{qV}{kT}} - 1)$$

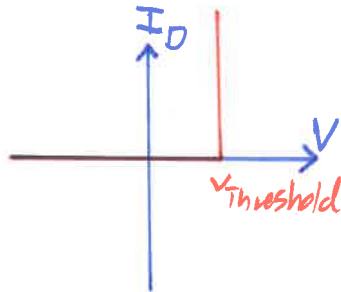


Assumed

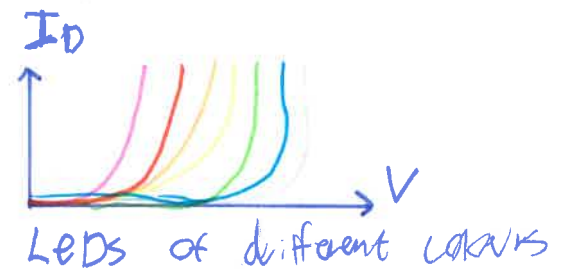


Transistor (not part of course)

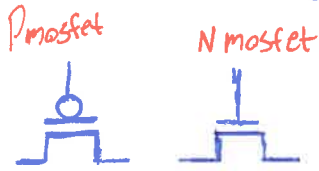gate $\begin{matrix} + \\ \text{Drain} \\ - \\ \text{Source} \end{matrix}$ If there is a potential at the gate current may flow from drain to source or vice versa.



Operational Amplifier



Amplifies Voltages, both up or down.

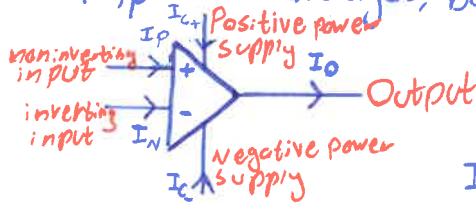

Currents going in and out of the amplifier sum up to zero.

$$I_p = I_n \approx 0 \Rightarrow I_{c+} + I_{c-} = I_o$$

All current comes from power supply

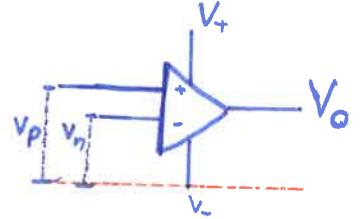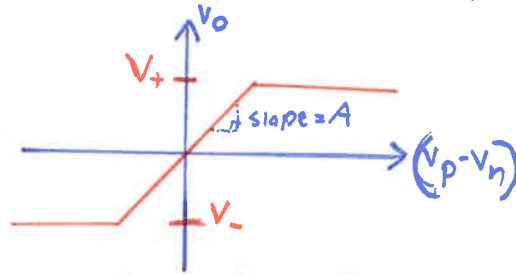


Negative Linear Saturation region Positive Saturation

Operational Amp. Analysis

- 1 check for negative feedback \Rightarrow linear region.
- 2 write KCL at negative input terminal.
- 3 solve KCL, Remember $V_p \approx V_n$ in the linear region
- 4 Compare V_{out} to the supply to determine saturation.

In the linear region:

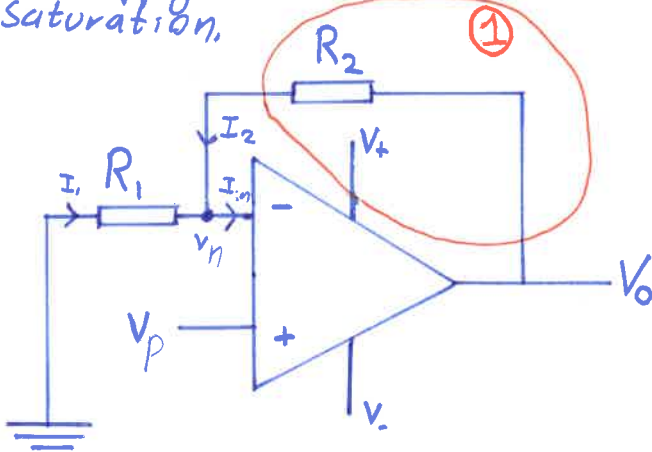$V_o = A(v_p - v_n)$ A is usually very large $\sim 10^4$
Negative feedback is used to stay in the very narrow linear region.



$$I_1 + I_2 = I_{in} \quad \{I_{in} = 0\}$$

$$I_1 + I_2 = 0$$

$$I_1 = \frac{0 - v_n}{R_1}; \quad I_2 = \frac{V_o - v_n}{R_2}$$

$$\frac{-v_n}{R_1} + \frac{V_o - v_n}{R_2} = 0 \quad \{v_n = V_p\}$$

$$\frac{V_o}{R_2} - V_p \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = 0$$

$$V_o = \left(1 + \frac{R_2}{R_1} \right) V_p$$

Determine value of R_2, R_1, V_p and solve V_o
determine the linear region

④

③

Inductance & Capacitance

Geometrical effects, cause delays in changes in voltage and current.

Capacitance: $Q = CV$ [F farad]

↳ Voltage created by separation of charges is proportional to capacitance.

Inductance: $\Phi_B = L \cdot I$ [H henry]

↳ Magnetic field created by a current is proportional to the Inductance.

Capacitor cont.

$I = C \cdot \frac{dV}{dt} \Rightarrow$ Current = 0 if V is constant

$V(t) = \frac{1}{C} \int_{t_0}^t (I \cdot dt) + V(t_0)$

total current flowing into capacitor.

$V(t) = V_0 \cdot e^{-\frac{t}{RC}}$ $RC = \tau$ } discharge towards zero

Between voltages

$V(t) = V(\infty) + (V(0) - V(\infty))e^{-\frac{t}{\tau}}$ } charge/discharge between voltages

~~$I_C(t) = \frac{V(t)}{R} = \frac{V_0}{R} e^{-\frac{t}{\tau}}$?~~

$P(t) = IV = \frac{V_0^2}{R} e^{-\frac{2t}{\tau}}$

In series: $\frac{1}{C_{tot}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$


In parallel: $C_{tot} = C_1 + C_2 + \dots$

$E = \frac{1}{2} CV^2$

Capacitor \parallel

A device designed to have a large capacitance.


$C = \frac{\epsilon A}{d}$

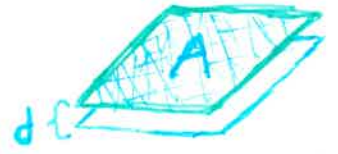

Induction \sim

A device designed to have a large Inductance.

$L = \mu_0 N^2 AL$

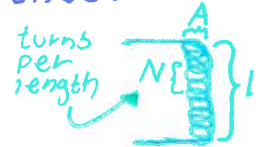

Inductor cont

$V = L \frac{dI}{dt} \Rightarrow$ Voltage drop (resistance) is zero if I is constant

$I(t) = \frac{1}{L} \int_{t_0}^t (v dt) + I(t_0)$

$I(t) = I(\infty) + (I(0) - I(\infty))e^{-\frac{t}{\tau}}$ $\tau = \frac{L}{R}$

$I(t) = I_0 e^{-\frac{t}{\tau}}$ } discharge towards zero

~~$V = IR = I_0 R e^{-\frac{t}{\tau}}$?~~

$P(t) = IV = I_0^2 R e^{-\frac{2t}{\tau}}$

In series: $L_{tot} = L_1 + L_2 + \dots$


In parallel: $\frac{1}{L_{tot}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots$

$E = \frac{1}{2} LI^2$

Sinusoidal Sources.

Voltage variations over time can be expressed by:

$$v(t) = V_m \sin(\omega t + \phi)$$

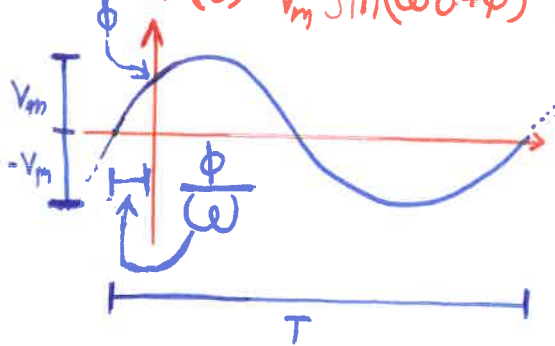

$$f = \frac{1}{T} \quad \omega = 2\pi f$$

Phasor Transform

writing sin & cos using e^{jx}

$$e^{jx} = \cos(x) + j\sin(x) \quad j = \sqrt{-1}$$

$$\Rightarrow \text{RE}(e^{jx}) = \cos(x)$$

$$\text{IM}(e^{jx}) = \sin(x)$$

This means:

$$I = I_m \cos(\omega t + \phi)$$

$$\Leftrightarrow \text{RE}\{I_m e^{j(\omega t + \phi)}\}$$

$$\Leftrightarrow \text{RE}\{I_m e^{j\phi} e^{j\omega t}\}$$

Phasor \hat{I}
Amplitude
Phase angle

RMS: Root Mean Squared

$$V_{\text{RMS}} = \frac{V_m}{\sqrt{2}} \rightarrow \text{only dependent on } V_m.$$

Implications:

$$V = IR \quad \text{---} \square \text{---} \quad V = L \frac{dI}{dt} \quad \text{---} \text{---} \text{---}$$

$$I = C \frac{dV}{dt} \quad \text{---} \text{---} \text{---}$$

not equal to zero

Impedance

Unit is ohm.

$$\hat{V} = Z \cdot \hat{I}$$

↑
impedance

only dependent on ω

Resistor \square


$$Z = R$$

Inductor $\text{---} \text{---} \text{---}$

$$Z_L = i\omega L$$

Capacitor $\text{---} \text{---} \text{---}$

$$Z_C = \frac{1}{i\omega C}$$

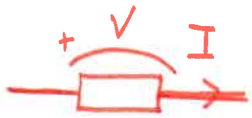

$$I = I_m \cos(\omega t + \phi)$$

$$\hat{I} = I_m e^{j\phi} = I_m \angle \phi$$

$$V = IR = R_m \cos(\omega t + \phi)$$

$$\vec{V} = R \hat{I}$$



$$\hat{I} = I_m \angle \phi$$

$$V = L \frac{dI}{dt} = L I_m (-\sin(\omega t + \phi)) \omega$$

$$= -\omega L I_m \sin(\omega t + \phi)$$

$$\hat{V} = -\omega L I_m \angle \phi - 90 = -\omega L I_m e^{j\phi} e^{-j\frac{\pi}{2}}$$

$$\hat{V} = i\omega L \hat{I}$$






$$\hat{V} = V_m \angle \phi$$

$$\hat{I} = C \frac{d\hat{V}}{dt} = C V_m (-\sin(\omega t + \phi)) \omega$$

$$= -\omega C V_m \sin(\omega t + \phi)$$

$$\Rightarrow \hat{I} = i\omega C \hat{V}$$




Filters

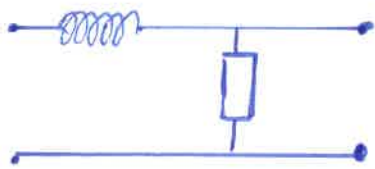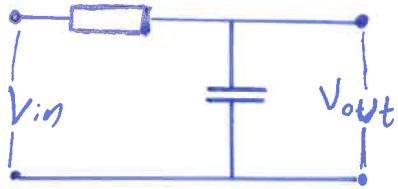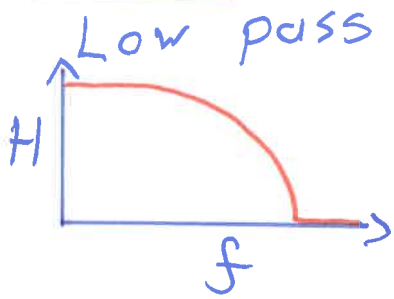

$$H = \frac{V_{out}}{V_{in}}$$

for capacitor

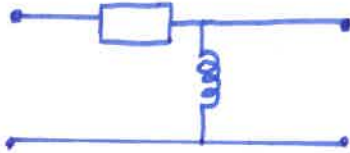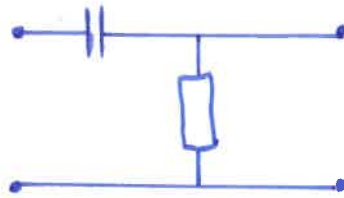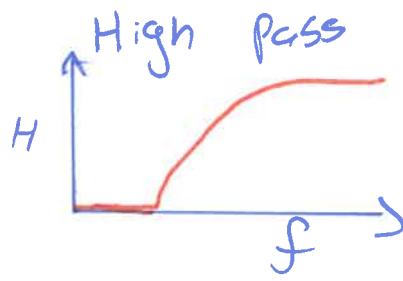
$$f_c = \frac{1}{RC} \cdot \frac{1}{2\pi}$$




$f_{cutoff} \Rightarrow$ frequency where $H = \frac{1}{\sqrt{2}}$

for Inductor
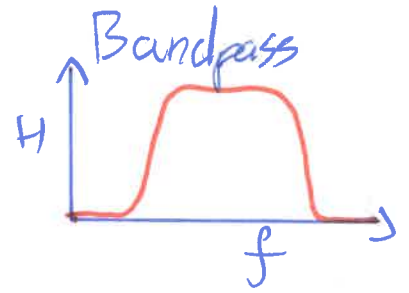
$$f_c = \frac{R}{L} \cdot \frac{1}{2\pi}$$



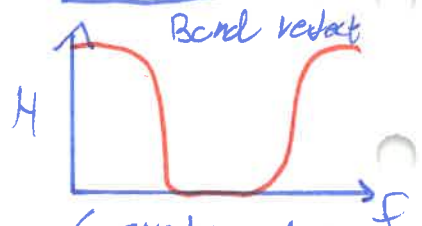Combination of a high and low pass in series.



Combination of high and low pass in parallel